

## **NORTH SOUTH UNIVERSITY**

**Department of Electrical & Computer Engineering**

### **Lab Report**

**Course Code:** EEE111L

**Course Title:** Analog Electronics

**Section:** 03

**Experiment No:** 05

**Experiment Name:** The input output characteristics of CE configuration of BJT

**Experiment Date:** 11<sup>th</sup> April 2021

**Date of Submission:** 25<sup>th</sup> April 2021

**Course Instructor:** Riasat Khan

**Submitted by Group 05**

1. MD Abu Sayed Fahim (1812534642)
2. Sifatulla (1813317642)
3. Rashedul Islam Hridoy (1812559642)
4. Md Shamim Hossain (1721886)

**Submitted to:** Fatema Zahra

Experiment No : 05

Name of the experiment : The input output characteristics of CE (Common emitter) configuration of BJT.

Objective : Study of the input output characteristics of CE (common emitter) configuration of BJT.

Theory : A transistor is a three terminal device. The terminals are base, emitter and collector. In CE configuration input voltage is applied between base and emitter terminals. Therefore, the emitter terminal is common to both input and output. So, for normal operation Base emitter junction is forward biased. as compared to CB arrangement  $I_B$  increases less rapidly with  $V_{BE}$ .

Therefore, input resistance of CE circuit is higher than CB circuit. There are three different currents ( $I_E$ ,  $I_B$ ,  $I_C$ ).

Here,  $I_E = I_B + I_C$  and current gain  $\frac{I_E}{I_B}$ .

The characteristics of transistor is measured by following two characteristic's curve.


**Input characteristics curve:** It is the same graph /curve that is found for a forward bias diode. Because, it's the curve between input current ( $I_B$ ) vs output voltage ( $V_{CE}$ ) for constant output voltage ( $V_E$ ).

**Output characteristic curve:** It is output current ( $I_C$ ) vs output voltage ( $V_{CE}$ ) for constant ( $I_B$ ). It has three region Saturation, Active, cut off. In Saturation region collector diode is not in reversed bias so,

here,  $V_{CE}$  is the rising part of the curve. When it becomes reverse biased the graph becomes horizontal. When,  $I_B = 0$  the collector curve is in Cutoff region where, transistor works as switch.

### Equipments and Components:

Serial	Component name	Specification	Quantity
1	Transistor	C828	1 piece
2	Resistor	100k $\Omega$ , 1k $\Omega$	1 piece each
3	Trainer board		1 unit
4	De power supply		1 unit
5	Digital multimeter (DMM)		1 unit
6	Chords and wire		as required

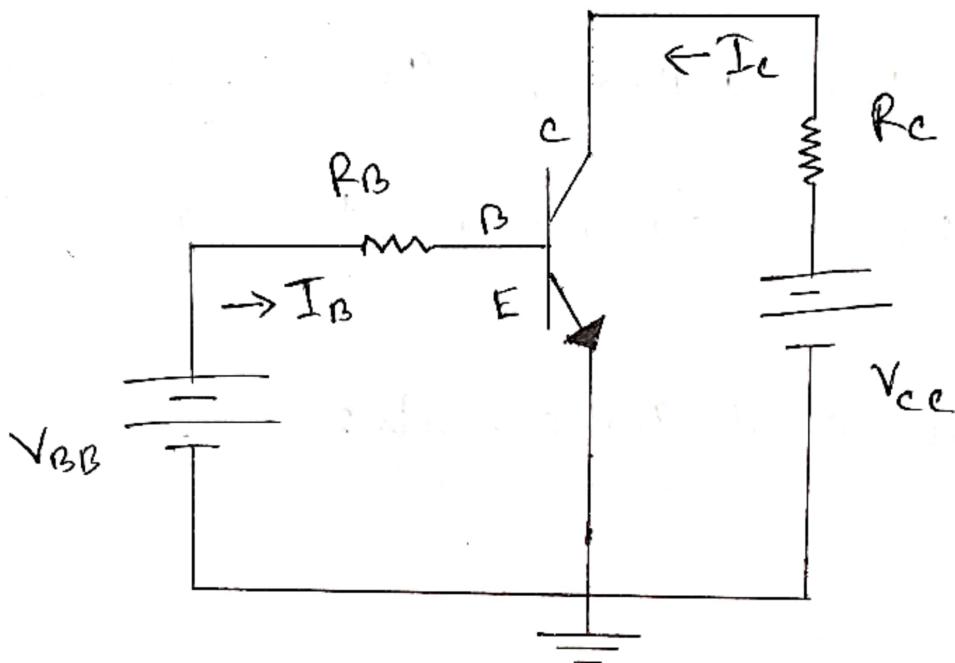Circuit Diagram :

## Data Collection :

Table ① Input characteristic of BJT


$V_{CE} = 1V$			$V_{CE} = 5V$	
$V_{BB}$ (v)	$V_{BE}$ (v)	$I_B = \frac{V_{RB}}{R_B}$ (mA)	$V_{BE}$ (v)	$I_B = \frac{V_{RB}}{R_B}$
0.1	0.10	0	0.11	0
0.3	0.21	0	0.24	0
0.5	0.46	0.10	0.48	0.10
0.7	0.50	5.7	0.57	1.0
1.0	0.62	3.7	0.62	3.6
2.0	0.63	13.2	0.66	13.3
3.0	0.63	23.6	0.67	22.6
4.0	0.64	35.0	0.68	33.1
5.0	0.64	43.7	0.68	43.1
7.0	0.64	64.0	0.68	63.6
9.0	0.64	83.4	0.68	83.6
10.0	0.65	93.9	0.68	93.8
12.0	0.65	114.0	0.68	114.0
14.0	0.65	133.7	0.69	133.4
16.0	0.65	153.4	0.69	153.9

Table (2) Output Characteristic of BJT

$I_B = 20 \text{ mA}$			$I_B = 30 \text{ mA}$	
$V_{CE} (\text{v})$	$V_{CE} (\text{v})$	$I_C = \frac{V_{RE}}{R_E} (\text{mA})$	$V_{CE} (\text{v})$	$I_C = \frac{V_{RE}}{R_E} (\text{mA})$
1.0	0.09	0.95	0.07	0.98
2.0	0.12	1.84	0.10	1.88
3.0	0.16	2.77	0.12	2.86
4.0	0.56	3.37	0.14	3.76
5.0	1.46	3.40	0.17	4.79
6.0	2.49	3.43	0.24	5.66
8.0	4.40	3.43	1.81	6.13
10.0	6.28	3.49	3.73	6.26
12.0	8.25	3.54	5.54	6.35
14.0	10.09	3.60	7.44	6.50
16.0	12.29	3.69	9.38	6.59
18.0	14.28	3.71	11.32	6.73
20.0	16.24	3.75	13.12	6.84
22.0	18.10	3.81	15.03	6.95
24.0	20.20	3.96	16.87	7.05
1	1	1	1	1

1

Roll No. ....

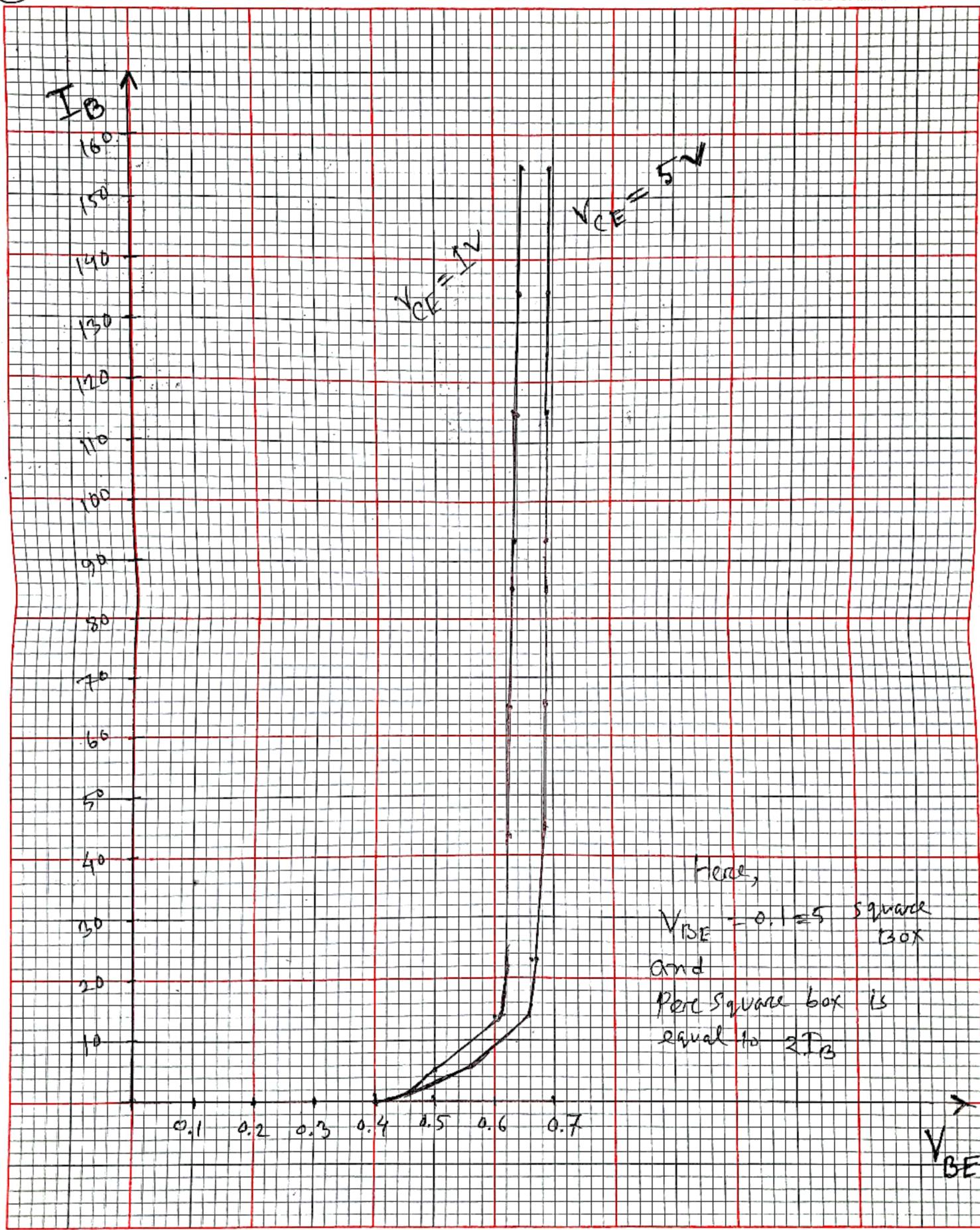

here,


 $V_{BE} = 0.1 \text{ V}$  square  
box

and

Per square box is  
equal to  $2T_B$

(2)

Roll No. ....

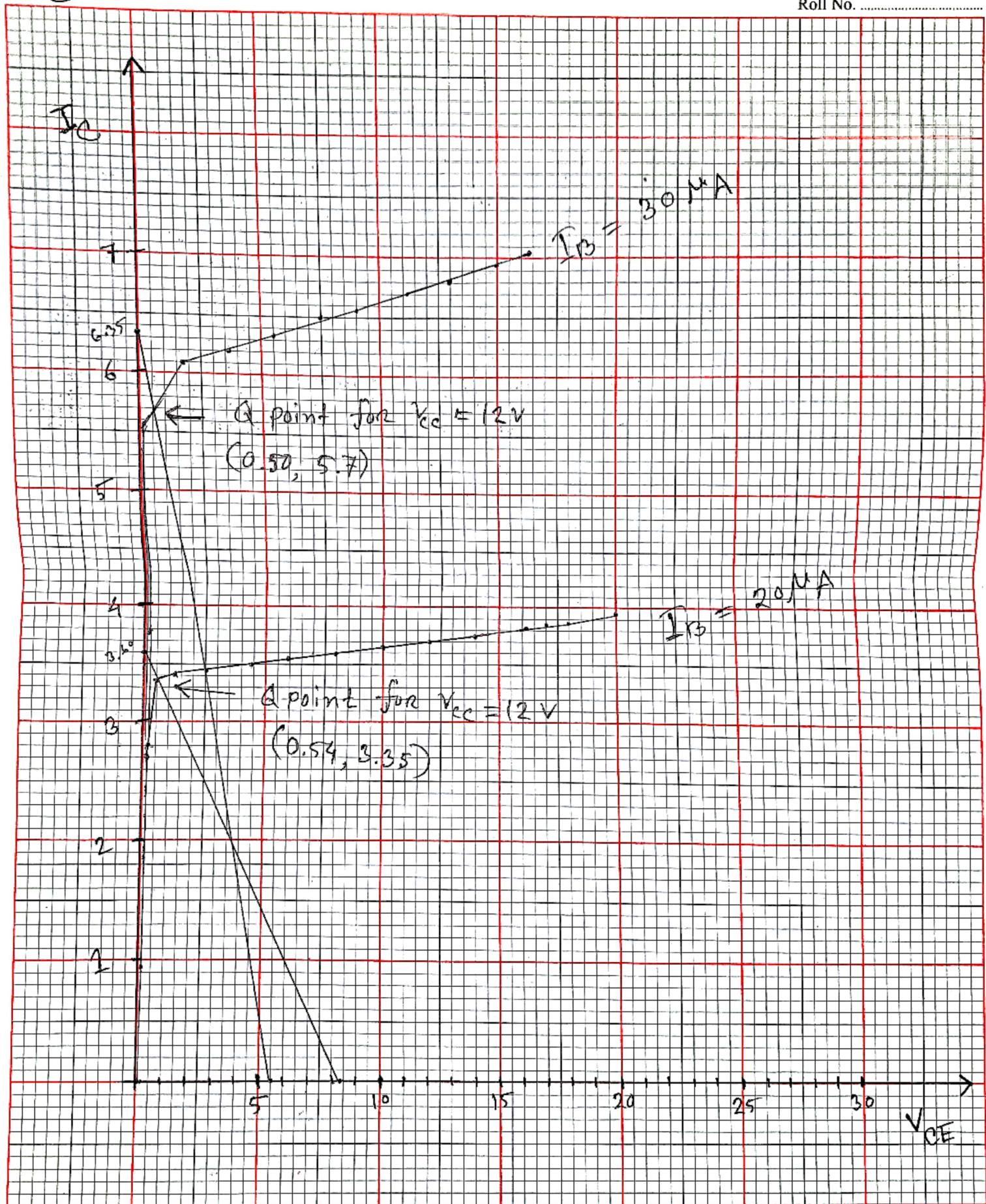

③ From table-2 output characteristic of

BJT we see  $V_{CE}$  is 1.96 volt when

$V_{CC}$  is 5 volt. When  $I_B = 20\text{mA}$

and for  $I_B = 30\text{mA}$   $V_{CE} = 1.81\text{ Volt}$  when

$V_{CC} = 7.0\text{ Volt}$ . As we know between

'0' and approximately 1. volt  $V_{CE}$  the

Region is called as Saturation Region.

So, for active region B we will consider

$V_{CE}$  after 1 volt.

$\beta$  table for  $I_B$  in active region:

$I_B = 20 \text{ mA}$			$I_B = 30 \text{ mA}$		
$V_{CE} (\text{V})$	$I_C (\text{mA})$	$\beta = \frac{I_C}{I_B}$	$V_{CE} (\text{V})$	$I_C (\text{mA})$	$\beta = \frac{I_C}{I_B}$
5.0	3.40	170	5.0	-	-
6.0	3.43	171.5	6.0	-	-
8.0	3.49	174.5	8.0	6.13	204.3
10.0	3.54	177	10.0	6.26	208.67
14.0	3.69	182	14.0	6.50	248.67
18.0	3.75	187.5	18.0	6.73	234.33
22.0	3.85	192.5	22.0	6.95	238.67
24.0	3.96	198	24.0	7.05	235

④ For  $V_{CC} = 12V$ , we drew the load line on the graph and we get two different co-ordinates for  $I_B = 20\text{mA}$  and  $30\text{mA}$  graph.

When  $I_B = 20\text{mA}$  graph Q point:  $(0.54, 3.35)$

when,  $I_B = 30\text{mA}$  graph Q point:  $(0.50, 5.7)$

## Discussion : The base current $I_B$

increases with the increases in the emitter-base voltage  $V_{BE}$  which is similar to the forward diode characteristic.

The value of the collector current  $I_C$  increased with the increase of  $V_{CE}$  at constant voltage. The value  $\beta$  also increases when  $V_{CE}$  falls. The  $I_C$  also decrease rapidly.

The collector-base junction of the transistor in saturation work as forward biased but in active region work as reverse biased.

# Group 05

Md Abu Sayed Fahim

1812534642

Sifatulla

1813317642

Rashedul Islam Hridoy

1812559642

Md Shamim Hossain

1721886

